

Table 1: Digital 2048 kHz Clock Interfaces

Pulse Shape	Signal Requirement	
Type of Interface	Coaxial Pair	Symmetrical Pair
Impedance	75Ω	120Ω
Max Peak Voltage (V)	1.5V	1.9V
Min Peak Voltage (V1)	0.75V	1.0V
Max Jitter at Output	(see Table 2)	

Table 2: Maximum Permissible Jitter at Synchronization Interfaces

Output Interfaces	Frequency Accuracy	Measurement Bandwidth, -3 dB Frequencies (Hz)	Peak-to-Peak Amplitude (Upp)
PRC	G.811	20–100k	0.05
SSU	G.812	20–100k	0.05
SEC	4.6ppm (refer to G.813)	20–100k	0.5
		49–100k	0.2
PDH Synchronization	±50ppm	20–100k	1.5
		18–100k	0.2


Note: For other specifications (i.e., noise tolerance at input ports), please refer to G.812 and G.813 for SSU and SEC, respectively.

Receive and Transmit of 2048kHz Clock

By configuring 82V2081 in “slicer” mode (R_MD[1:0] = 00), the receiver will work in slicer mode. The 2.048MHz clock can be received and output at RDP/RDN. In order to transmit the clock, the following circuit in Figure 1 is proposed.


The transmitter needs to be external for G.703 Section 13 support. For the external circuit to work, 82V2081's own transmitter needs to be in high impedance to avoid signal conflict. That can be realized by setting T_OFF = 1.

External circuit in Figure 1 is shown below. The circuitry consists of discrete components. The 2.048MHz is a 3.3V CMOS clock input signal. The transistor (M1) is used to boost transmitter's driving capability into the transmission lines. The power for the transistor can be 3.3V or 2.5V. The selection of 3.3V or 2.5V is discussed in the following section. The transformer is modeled from our suggested turn ratio = 1:2 transformers (refer to AN-377).

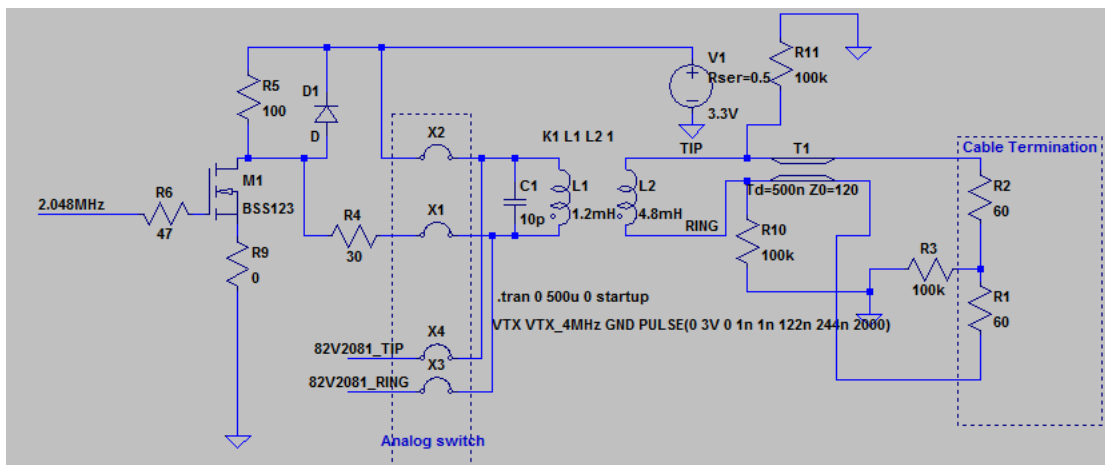Figure 1. Proposed External Transmitter Circuit


Transmitted pulses are analyzed with the following simulation results. [Figure 2](#) shows the transmitted pulses with 3.3V power supply for the transistor (M1). The total pulse amplitude is 4.1V with 2.4V DC offset. The net signal amplitude is 1.7V, meeting pulse amplitude requirement for twisted-pair transmission (refer to [Table 1](#) above).

Figure 2. Transmitted Pulses with 3.3V

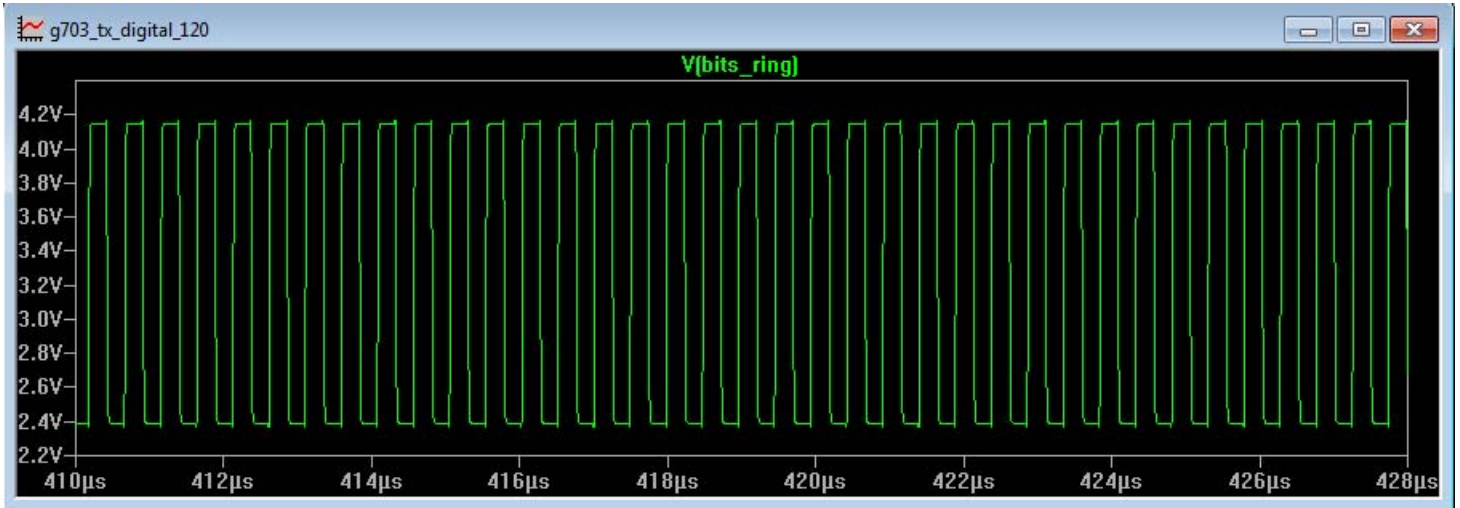

[Figure 3](#) shows the lower transmitted pulse amplitude with transistor power supply of 2.5V. In this condition, total signal amplitude is close to 3.2V with a DC offset 1.8V, leaving the net signal amplitude of about 1.4V, also meeting required signal level ([Table 1](#)).

Figure 3. Transmitted Pulses with 2.5V

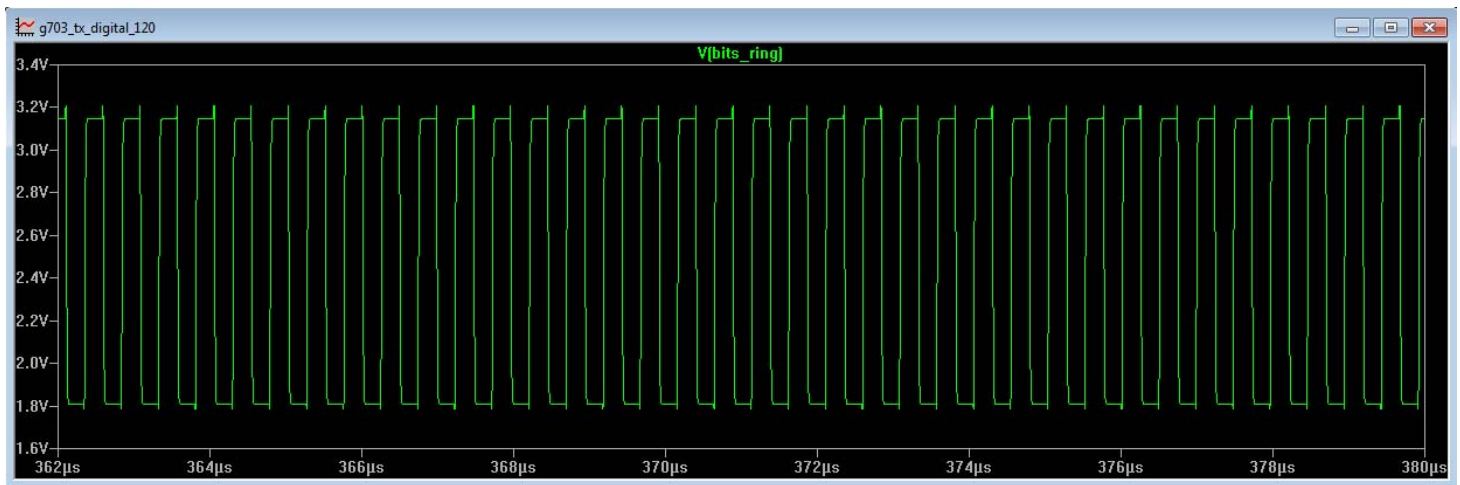

X1~X4 are 4 analog switches. Any STDP with low R_{on} can be used. Analog switches are used to isolate the 82V2081's own circuit from external transmitter. When 2.5V is used as the transistor power supply, the transmitted pulses have an overall amplitude of 3.2V, which will not conduct the ESD diodes used in the circuit as a protection diodes. In this condition, X3 and X4 are not needed.

Circuit Implementations

The circuit uses a transistor, a 1:2 transformer and a few analog switches. The transistor used in the example is BSS123. Other transistors can be used with similar specifications. The transformer can be selected from IDT's transformer selection guide [AN-377](#) with a turn ratio of 1:2. R5 is a current-limiting resistor. The power rating for this resistor should be $\geq 0.1W$. R4 is the termination impedance. For 120 Ω twisted-pair transmission line, $R4 = 30\Omega$. For 75 Ω coax transmission, it is 18.75 Ω .



Corporate Headquarters
6024 Silver Creek Valley Road
San Jose, CA 95138 USA

Sales
1-800-345-7015 or 408-284-8200
Fax: 408-284-2775
www.IDT.com

Tech Support
email: clocks@idt.com

DISCLAIMER Integrated Device Technology, Inc. (IDT) and its subsidiaries reserve the right to modify the products and/or specifications described herein at any time and at IDT's sole discretion. All information in this document, including descriptions of product features and performance, is subject to change without notice. Performance specifications and the operating parameters of the described products are determined in the independent state and are not guaranteed to perform the same way when installed in customer products. The information contained herein is provided without representation or warranty of any kind, whether express or implied, including, but not limited to, the suitability of IDT's products for any particular purpose, an implied warranty of merchantability, or non-infringement of the intellectual property rights of others. This document is presented only as a guide and does not convey any license under intellectual property rights of IDT or any third parties.

IDT's products are not intended for use in applications involving extreme environmental conditions or in life support systems or similar devices where the failure or malfunction of an IDT product can be reasonably expected to significantly affect the health or safety of users. Anyone using an IDT product in such a manner does so at their own risk, absent an express, written agreement by IDT.

Integrated Device Technology, IDT and the IDT logo are registered trademarks of IDT. Product specification subject to change without notice. Other trademarks and service marks used herein, including protected names, logos and designs, are the property of IDT or their respective third party owners.

Copyright ©2015 Integrated Device Technology, Inc.. All rights reserved.